

EE446 - Experiment 1

Preliminary Work

1.2.1) Constant Value Generator

```

1. module constantValueGenerator
2.     # (parameter W = 3, C = 9) (bus_out);
3.
4.     output wire [W-1:0] bus_out;
5.
6.     assign bus_out = C;
7. endmodule

```

1.2.2) Decoder

.v file:

```

1. module Decoder2to4 (input0, input1, o0, o1, o2, o3);
2.
3.     input wire input0, input1;
4.     output wire o0, o1, o2, o3;
5.
6.     assign o0 = ~input0 & ~input1;
7.     assign o1 = input0 & ~input1;
8.     assign o2 = ~input0 & input1;
9.     assign o3 = input0 & input1;
10.
11. endmodule
12.

```

testbench:

```

1. module Decoder2to4_tb ();
2.     wire ou0, ou1, ou2, ou3;
3.     reg in0, in1;
4.     Decoder2to4 DUT(in0, in1, ou0, ou1, ou2, ou3);
5.     reg [5:0] mem [3:0];
6.     integer i;
7.
8.     initial begin
9.         $readmemb("C:/Users/AhmetSalih/Desktop/EE446_Desktop/test_vectors/Decoder_tb
_vector.txt" , mem);
10.        #1000;
11.    end
12.    always @(*) begin
13.        for(i=0;i<4;i=i+1) begin
14.            in0 = mem[i][4];
15.            in1 = mem[i][5];
16.            #10;
17.            if({ou3,ou2,ou1,ou0} == mem[i][3:0])
18.                $display ("No Error in %1d th row", i+1);
19.            else
20.                $display ("Error in %1d th row", i+1);
21.        end
22.    end
23. endmodule

```

testvector:

```
1. 00_0001
2. 01_0010
3. 10_0100
4. 11_1000
```

1.2.3) Multiplexers

2x1 .v file:

```
1. module Mux2to1
2.     #(parameter W = 3) (i0, i1, select, out);
3.
4.     input [W-1:0] i0, i1;
5.     input select;
6.     output [W-1:0] out;
7.
8.     assign out = (select) ? i1 : i0;
9.
10. endmodule
```

2x1 testbench:

```
1. module Mux2to1_tb
2.     #(parameter W = 2) ();
3.
4.     reg [W-1:0] i0, i1;
5.     reg select;
6.     wire [W-1:0] out;
7.
8.     reg [6:0] mem [1:0];
9.
10.    Mux2to1 DUT(i0,i1,select,out);
11.    integer i;
12.
13.    initial begin
14.        $readmemb("C:/Users/AhmetSalih/Desktop/EE446_Desktop/test_vectors/Mux2to1_tb_vector.txt", mem);
15.        #1000;
16.    end
17.    always @(*) begin
18.        for(i=0;i<2;i=i+1) begin
19.            i0 = mem[i][4:3];
20.            i1 = mem[i][6:5];
21.            select = mem[i][2];
22.            #10;
23.            if(out == mem[i][1:0])
24.                $display ("No Error in %1d th row", i+1);
25.            else
26.                $display ("Error in %1d th row", i+1);
27.        end
28.    end
29. endmodule
```

2x1 test vector:

```

1. //in1_in0_select_out
2. 10_11_0_11
3. 10_11_1_10

```

4x1 .v file:

```

1. module Mux4to1
2.     #(parameter W = 2) (in0,in1,in2,in3,select,out);
3.
4.     input wire [W-1:0] in0,in1,in2,in3;
5.     input wire [1:0] select;
6.     output reg [W-1:0] out;
7.
8.     always @* begin
9.         case(select)
10.            2'b00: out=in0;
11.            2'b01: out=in1;
12.            2'b10: out=in2;
13.            2'b11: out=in3;
14.        endcase
15.    end
16.
17. endmodule

```

4x1 testbench:

```

1. module Mux4to1_tb
2.     #(parameter W = 2) ();
3.
4.     reg [W-1:0] i0, i1, i2, i3;
5.     reg [1:0] select;
6.     wire [W-1:0] out;
7.
8.     reg [11:0] mem [3:0];
9.
10.    Mux4to1 DUT(i0,i1,i2,i3,select,out);
11.    integer i;
12.
13.    initial begin
14.        $readmemb("C:/Users/AhmetSalih/Desktop/EE446_Desktop/test_vectors/Mux4to1_tb_vector.txt" , mem);
15.        #1000;
16.    end
17.    always @(*) begin
18.        for(i=0;i<4;i=i+1) begin
19.            i0 = mem[i][11:10];
20.            i1 = mem[i][9:8];
21.            i2 = mem[i][7:6];
22.            i3 = mem[i][5:4];
23.            select = mem[i][3:2];
24.            #10;
25.            if(out == mem[i][1:0])
26.                $display ("No Error in %1d th row", i+1);
27.            else
28.                $display ("Error in %1d th row", i+1);
29.        end
30.    end
31. endmodule

```

4x1 test vector:

```

1. //in0_in1_in2_in3_select_out
2. 00_01_10_11_00_00
3. 00_01_10_11_01_01
4. 00_01_10_11_10_10
5. 00_01_10_11_11_11

```

1.2.4) ALU

.v file:

```

1. module ALU
2.     #(parameter W = 5) (SrcA, SrcB, Control, Result, CO, OVF, N, Z);
3.
4.     //W-bit Inputs
5.     input wire [W-1:0] SrcA, SrcB;
6.     //3 bit Control Signal
7.     input [2:0] Control;
8.     //N-bit Result
9.     output reg [W-1:0] Result;
10.    //Status Flags
11.    output reg CO, OVF, N, Z;
12.
13.    reg [W-1:0] temp_add;
14.
15.
16.    always @(*) begin
17.        case(Control)
18.            3'b000: begin //Addition
19.                {CO,Result} = {1'b0,SrcA} + {1'b0,SrcB};
20.                if((SrcA[W-1] == SrcB[W-1]) && (Result[W-1]!=SrcA[W-
21.                1])) OVF=1'b1;
22.                else OVF=1'b0;
23.                if(Result[W-1] == 1'b1) N=1'b1;
24.                else N=1'b0; //Negative flag
25.                N = N & (~OVF); //When OVF=1 N should be 0
26.                if(Result == 0) Z=1'b1;
27.                else Z=1'b0;
28.            end//End of Addition case
29.            3'b001: begin //SubtractionAB
30.                {CO,Result} = {1'b0,SrcA} - {1'b0,SrcB};
31.                if((SrcA[W-1] == ~SrcB[W-1]) && (Result[W-1]!=SrcA[W-
32.                1])) OVF=1'b1;
33.                else OVF=1'b0;
34.                //If Result is a different sign then the inputs then overflo
35.                w.
36.                if(Result[W-1] == 1'b1) N=1'b1;
37.                else N=1'b0; //Negative flag
38.                N = N & (~OVF); //When OVF=1 N should be 0
39.                if(Result == 0) Z=1'b1;
40.                else Z=1'b0;
41.            end // End of SubtractionAB
42.            3'b010: begin //SubtractionBA
43.                {CO,Result} = {1'b0,SrcB} - {1'b0,SrcA};
44.                if((~SrcA[W-1] == SrcB[W-1]) && (Result[W-1]!=SrcB[W-
45.                1])) OVF=1'b1;
46.                else OVF=1'b0;
47.                if(Result[W-1] == 1'b1) N=1'b1;
48.                else N=1'b0; //Negative flag
49.                N = N & (~OVF); //When OVF=1 N should be 0
50.                if(Result == 0) Z=1'b1;

```

```

47.         else Z=1'b0;
48.     end // End of SubtractionBA
49.     3'b011: begin //BitClear
50.         Result = SrcA & (~SrcB);
51.         if(Result == 0) Z=1'b1;
52.         else Z=1'b0;
53.         if(Result[W-1] == 1'b1) N=1'b1;
54.         else N=1'b0; //Negative flag
55.         CO=1'b0;
56.         OVF=1'b0;
57.     end//End of BitClear
58.     3'b100: begin //AND
59.         Result = SrcA & SrcB;
60.         if(Result == 0) Z=1'b1;
61.         else Z=1'b0;
62.         if(Result[W-1] == 1'b1) N=1'b1;
63.         else N=1'b0; //Negative flag
64.         CO=1'b0;
65.         OVF=1'b0;
66.     end // End of AND
67.     3'b101: begin //OR
68.         Result = SrcA | SrcB;
69.         if(Result == 0) Z=1'b1;
70.         else Z=1'b0;
71.         if(Result[W-1] == 1'b1) N=1'b1;
72.         else N=1'b0; //Negative flag
73.         CO=1'b0;
74.         OVF=1'b0;
75.     end // End of OR
76.     3'b110: begin //EXOR
77.         Result = SrcA ^ SrcB;
78.         if(Result == 0) Z=1'b1;
79.         else Z=1'b0;
80.         if(Result[W-1] == 1'b1) N=1'b1;
81.         else N=1'b0; //Negative flag
82.         CO=1'b0;
83.         OVF=1'b0;
84.     end //End of EXOR
85.     3'b111: begin //EXNOR
86.         Result = ~(SrcA ^ SrcB);
87.         if(Result == 0) Z=1'b1;
88.         else Z=1'b0;
89.         if(Result[W-1] == 1'b1) N=1'b1;
90.         else N=1'b0; //Negative flag
91.         CO=1'b0;
92.         OVF=1'b0;
93.     end //End of EXNOR
94. endcase
95. end
96.
97. endmodule

```

testbench:

```

1. module ALU_tb
2.     #(parameter W=5) ();
3.
4.     //W-bit Inputs
5.     reg [W-1:0] SrcA, SrcB;
6.     //3 bit Control Signal
7.     reg [2:0] Control;
8.     //N-bit Result
9.     wire [W-1:0] Result;
10.    //Status Flags

```

```

11.    wire CO, OVF, N, Z;
12.
13.    reg [21:0] mem [12:0];
14.
15.    ALU DUT (SrcA, SrcB, Control, Result, CO, OVF, N, Z);
16.
17.    integer i;
18.
19.    initial begin
20.        $readmemb("C:/Users/AhmetSalih/Desktop/EE446_Desktop/test_vectors/ALU_tb_vector.txt", mem);
21.        #1000;
22.    end
23.    always @*
24.    begin
25.        for(i=0;i<13;i=i+1) begin
26.            SrcA = mem[i][21:17];
27.            SrcB = mem[i][16:12];
28.            Control = mem[i][11:9];
29.            #10;
30.            if({Result,CO,OVF,N,Z} == mem[i][8:0])
31.                $display ("No Error in %1d th row", i+1);
32.            else
33.                $display ("Error in %1d th row", i+1);
34.        end
35.    end
36. endmodule

```

ALU testvector:

```

1.  //input1_input2_Control_Result_CO,OVF,N,Z
2.  00111_00101_000_01100_0000
3.  00111_00101_001_00010_0000
4.  00111_00101_010_11110_1010
5.  00111_00101_011_00010_0000
6.  00111_00101_100_00101_0000
7.  00111_00101_101_00111_0000
8.  00111_00101_110_00010_0000
9.  00111_00101_111_11101_0010
10. //Zero detection test
11. 00111_00111_001_00000_0001
12. //Overflow Detection Test in Addition
13. 01101_01001_000_10110_0100
14. 10011_10101_000_01000_1100
15. 01110_11000_000_00110_1000
16. //Overflow Detection Test in Subtraction
17. 01101_10011_001_11010_1100

```

1.2.5) Registers:

Simple Register .v file:

```

1. module Reg_Simple
2.     #(parameter W=5) (clk, reset, data, out);
3.
4.     input wire clk,reset;
5.     input wire [W-1:0] data;
6.     output reg [W-1:0] out;
7.
8.     always @(posedge clk) begin
9.         if(reset==1'b1) out <= 0;

```

```

10.         else out <= data;
11.     end
12.
13. endmodule

```

Simple Register testbench:

```

1. module Reg_Simple_tb
2.     #(parameter W=5)();
3.
4.     reg clk,reset;
5.     reg [W-1:0] data;
6.     wire [W-1:0] out;
7.
8.     reg [10:0] mem [3:0];
9.
10.    Reg_Simple DUT (clk, reset, data, out);
11.
12.    integer i,j;
13.
14.    initial begin
15.        clk=0;
16.        $readmemb("C:/Users/AhmetSalih/Desktop/EE446_Desktop/test_vectors/Reg_Simple
17.        _tb_vector.txt" , mem);
18.        #1000;
19.    end
20.    always @* begin
21.        for(j=0;j<100;j=j+1) begin
22.            clk = clk ^ 1'b1;
23.            #5;
24.            //For now the frequency is too high but it's just for simulation
25.        end
26.    end
27.    always @*
28.    begin
29.        for(i=0;i<4;i=i+1) begin
30.            reset = mem[i][10];
31.            data = mem[i][9:5];
32.            #13;
33.            if(out == mem[i][4:0])
34.                $display ("No Error in %1d th row", i+1);
35.            else
36.                $display ("Error in %1d th row", i+1);
37.        end
38.    end
39. endmodule

```

Simple Register testvector:

```

1. //reset_data_out
2. 0_11010_11010
3. 0_10011_10011
4. 0_00001_00001
5. 1_11010_00000

```

Register with WE .v file:

```

1. module Reg_WE
2.     #(parameter W=5) (clk, reset, we, data, out);
3.
4.     input wire clk,reset,we;

```

```

5.     input wire [W-1:0] data;
6.     output reg [W-1:0] out;
7.
8.     always @(posedge clk) begin
9.         if(reset==1'b1) out <= 0;
10.        else begin
11.            if(we == 1'b1) out <= data;
12.        end
13.    end
14.
15. endmodule

```

Reg_WE testbench:

```

1. module Reg_WE_tb
2.     #(parameter W=5)();
3.
4.     reg clk,reset,we;
5.     reg [W-1:0] data;
6.     wire [W-1:0] out;
7.
8.     reg [11:0] mem [5:0];
9.
10.    Reg_WE DUT (clk, reset, we, data, out);
11.
12.    integer i,j;
13.
14.    initial begin
15.        clk=0;
16.        $readmemb("C:/Users/AhmetSalih/Desktop/EE446_Desktop/test_vectors/Reg_WE_tb_
vector.txt" , mem);
17.        #1000;
18.    end
19.    always @* begin
20.        for(j=0;j<100;j=j+1) begin
21.            clk = clk ^ 1'b1;
22.            #5;
23.            //For now the frequency is too high but it's just for simulation
24.        end
25.    end
26.    always @*
27.    begin
28.        for(i=0;i<6;i=i+1) begin
29.            reset = mem[i][11];
30.            we = mem[i][10];
31.            data = mem[i][9:5];
32.            #10;
33.            if(out == mem[i][4:0])
34.                $display ("No Error in %1d th row", i+1);
35.            else
36.                $display ("Error in %1d th row", i+1);
37.        end
38.    end
39. endmodule

```

Reg_WE testvector:

```

1. //reset_we_data_out
2. 0_1_11010_11010
3. 0_0_10011_11010
4. 0_1_00001_00001
5. 1_0_11010_00000

```



```
6. 0_1_11011_11011
7. 1_1_10011_00000
```

Shift Register .v file:

```
1. module Reg_Shift
2.     #(parameter W = 5) (clk, reset, ps_select, lr_select, data, input_left, input_right, out);
3.
4.     input wire clk, reset, ps_select, lr_select;
5.     input wire [W-1:0] data;
6.     input wire input_left, input_right;
7.
8.     output reg [W-1:0] out;
9.
10.    always @(posedge clk) begin
11.        if(reset==1) out<=0; //Synchronous reset
12.        else begin
13.            if(ps_select==1) begin
14.                out <= data; //If Parallel/Serial select=1 then load parallel data
15.            end
16.            else begin //Otherwise check for left/right shift signal
17.                if(lr_select == 1) begin //if lr=1 shift right
18.                    out <= {input_left, out[W-1:1]};
19.                end
20.                else begin //lr=0 so shift left
21.                    out <= {out[W-2:0], input_right};
22.                end
23.            end
24.        end
25.    end
26. endmodule
```

Shift Register testbench:

```
1. module Reg_Shift_tb
2.     #(parameter W=5)();
3.
4.     reg clk, reset, ps_select, lr_select, input_left, input_right;
5.     reg [W-1:0] data;
6.     wire [W-1:0] out;
7.
8.     reg [14:0] mem [6:0];
9.
10.    Reg_Shift DUT (clk, reset, ps_select, lr_select, data, input_left, input_right, out);
11.
12.    integer i, j;
13.
14.    initial begin
15.        clk=0;
16.        $readmemb("C:/Users/AhmetSalih/Desktop/EE446_Desktop/test_vectors/lab1_registerfile_tb_vector.txt" , mem);
17.        #1000;
18.    end
19.    always @* begin
20.        for(j=0; j<100; j=j+1) begin
21.            clk = clk ^ 1'b1;
22.            #5;
23.            //For now the frequency is too high but it's just for simulation
24.        end
25.    end
```



```
26.    always @*
27.    begin
28.        for(i=0;i<7;i=i+1) begin
29.            reset = mem[i][14];
30.            ps_select = mem[i][13];
31.            lr_select = mem[i][12];
32.            input_left = mem[i][11];
33.            input_right = mem[i][10];
34.            data = mem[i][9:5];
35.            #10;
36.            if(out == mem[i][4:0])
37.                $display ("No Error in %1d th row", i+1);
38.            else
39.                $display ("Error in %1d th row", i+1);
40.        end
41.    end
42. endmodule
```

Reg_Shift testvector:

```
1. //reset_pssselect,lrselect_inputleft,inputright_data_out
2. 0_10_11_11010_11010
3. 0_01_10_00011_11101
4. 0_01_00_00101_01110
5. 1_11_01_11010_00000
6. 0_11_10_11011_11011
7. 0_00_00_10011_10110
8. 0_00_01_11111_01101
```

1.3) Register File

Hand drawn schematics:

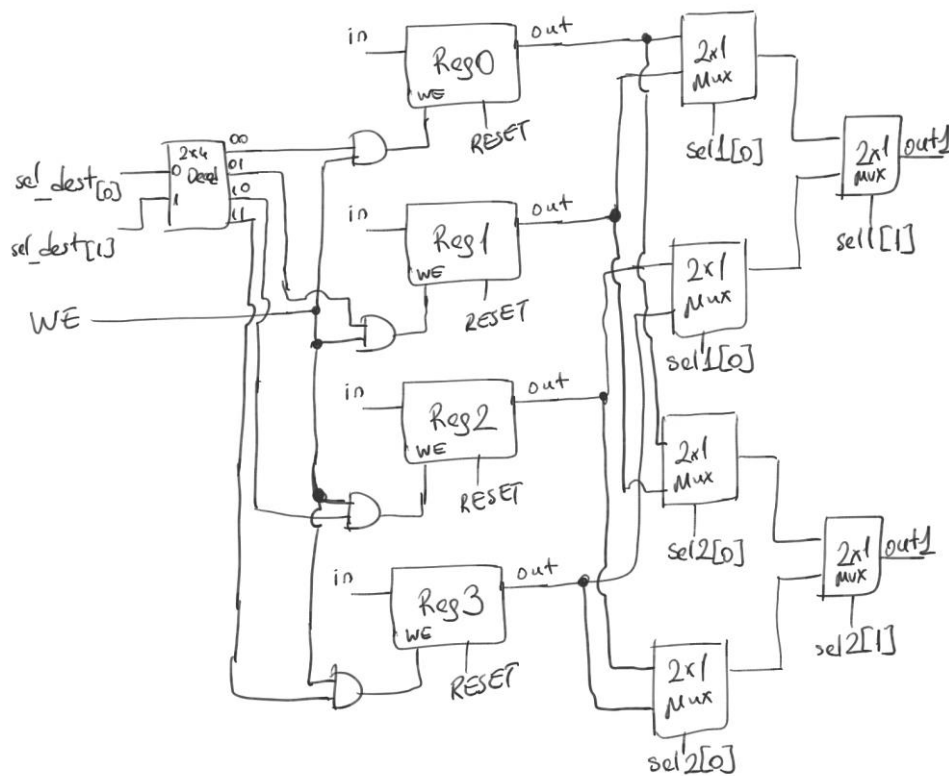 

.v file:

```

1. // Copyright (C) 1991-2016 Altera Corporation. All rights reserved.
2. // Your use of Altera Corporation's design tools, logic functions
3. // and other software and tools, and its AMPP partner logic
4. // functions, and any output files from any of the foregoing
5. // (including device programming or simulation files), and any
6. // associated documentation or information are expressly subject
7. // to the terms and conditions of the Altera Program License
8. // Subscription Agreement, the Altera Quartus Prime License Agreement,
9. // the Altera MegaCore Function License Agreement, or other
10. // applicable license agreement, including, without limitation,
11. // that your use is for the sole purpose of programming logic
12. // devices manufactured by Altera and sold by Altera or its
13. // authorized distributors. Please refer to the applicable
14. // agreement for further details.
15.
16. // PROGRAM      "Quartus Prime"
17. // VERSION      "Version 16.0.0 Build 211 04/27/2016 SJ Lite Edition"
18. // CREATED      "Tue Mar 27 03:01:29 2018"
19.
20. module lab1_registerfile
21. #(parameter W = 8)
22. (
23.     we,
24.     clk,
25.     reset,
26.     in,
27.     sel1,
28.     sel2,
29.     sel_dest,
30.     out1,
31.     out2
32. );
33.
34.
35. input wire  we;
36. input wire  clk;
37. input wire  reset;
38. input wire [W-1:0] in;
39. input wire [W-1:0] sel1;
40. input wire [1:0] sel2;
41. input wire [1:0] sel_dest;
42. output wire [W-1:0] out1;
43. output wire [W-1:0] out2;
44.
45. wire      SYNTHESIZED_WIRE_0;
46. wire      SYNTHESIZED_WIRE_1;
47. wire      SYNTHESIZED_WIRE_2;
48. wire      SYNTHESIZED_WIRE_3;
49. wire      SYNTHESIZED_WIRE_4;
50. wire      SYNTHESIZED_WIRE_5;
51. wire [W-1:0] SYNTHESIZED_WIRE_20;
52. wire [W-1:0] SYNTHESIZED_WIRE_21;
53. wire [W-1:0] SYNTHESIZED_WIRE_22;
54. wire [W-1:0] SYNTHESIZED_WIRE_23;
55. wire [W-1:0] SYNTHESIZED_WIRE_10;
56. wire [W-1:0] SYNTHESIZED_WIRE_11;
57. wire [W-1:0] SYNTHESIZED_WIRE_14;
58. wire [W-1:0] SYNTHESIZED_WIRE_15;
59. wire      SYNTHESIZED_WIRE_18;
60. wire      SYNTHESIZED_WIRE_19;
61.
62.

```

```

63.
64.
65.
66. Decoder2to4 b2v_inst(
67.     .input0(sel_dest[0]),
68.     .input1(sel_dest[1]),
69.     .o0(SYNTHESIZED_WIRE_2),
70.     .o1(SYNTHESIZED_WIRE_3),
71.     .o2(SYNTHESIZED_WIRE_4),
72.     .o3(SYNTHESIZED_WIRE_5));
73.
74.
75. Reg_WE b2v_inst10(
76.     .clk(clk),
77.     .reset(reset),
78.     .we(SYNTHESIZED_WIRE_0),
79.     .data(in),
80.     .out(SYNTHESIZED_WIRE_22));
81.     defparam b2v_inst10.W = W;
82.
83.
84. Reg_WE b2v_inst11(
85.     .clk(clk),
86.     .reset(reset),
87.     .we(SYNTHESIZED_WIRE_1),
88.     .data(in),
89.     .out(SYNTHESIZED_WIRE_23));
90.     defparam b2v_inst11.W = W;
91.
92. assign SYNTHESIZED_WIRE_18 = we & SYNTHESIZED_WIRE_2;
93.
94. assign SYNTHESIZED_WIRE_19 = we & SYNTHESIZED_WIRE_3;
95.
96. assign SYNTHESIZED_WIRE_0 = we & SYNTHESIZED_WIRE_4;
97.
98. assign SYNTHESIZED_WIRE_1 = we & SYNTHESIZED_WIRE_5;
99.
100.
101.     Mux2to1 b2v_inst2(
102.         .select(sel1[0]),
103.         .i0(SYNTHESIZED_WIRE_20),
104.         .i1(SYNTHESIZED_WIRE_21),
105.         .out(SYNTHESIZED_WIRE_10));
106.     defparam b2v_inst2.W = W;
107.
108.
109.     Mux2to1 b2v_inst3(
110.         .select(sel1[0]),
111.         .i0(SYNTHESIZED_WIRE_22),
112.         .i1(SYNTHESIZED_WIRE_23),
113.         .out(SYNTHESIZED_WIRE_11));
114.     defparam b2v_inst3.W = W;
115.
116.
117.     Mux2to1 b2v_inst4(
118.         .select(sel1[1]),
119.         .i0(SYNTHESIZED_WIRE_10),
120.         .i1(SYNTHESIZED_WIRE_11),
121.         .out(out1));
122.     defparam b2v_inst4.W = W;
123.
124.
125.     Mux2to1 b2v_inst5(
126.         .select(sel2[0]),
127.         .i0(SYNTHESIZED_WIRE_20),
128.         .i1(SYNTHESIZED_WIRE_21),

```

```

129.         .out(SYNTHESIZED_WIRE_14));
130.         defparam    b2v_inst5.W = W;
131.
132.
133.         Mux2to1 b2v_inst6(
134.             .select(sel2[1]),
135.             .i0(SYNTHESIZED_WIRE_14),
136.             .i1(SYNTHESIZED_WIRE_15),
137.             .out(out2));
138.         defparam    b2v_inst6.W = W;
139.
140.
141.         Mux2to1 b2v_inst7(
142.             .select(sel2[0]),
143.             .i0(SYNTHESIZED_WIRE_22),
144.             .i1(SYNTHESIZED_WIRE_23),
145.             .out(SYNTHESIZED_WIRE_15));
146.         defparam    b2v_inst7.W = W;
147.
148.
149.         Reg_WE b2v_inst8(
150.             .clk(clk),
151.             .reset(reset),
152.             .we(SYNTHESIZED_WIRE_18),
153.             .data(in),
154.             .out(SYNTHESIZED_WIRE_20));
155.         defparam    b2v_inst8.W = W;
156.
157.
158.         Reg_WE b2v_inst9(
159.             .clk(clk),
160.             .reset(reset),
161.             .we(SYNTHESIZED_WIRE_19),
162.             .data(in),
163.             .out(SYNTHESIZED_WIRE_21));
164.         defparam    b2v_inst9.W = W;
165.
166.
167.         // Copyright (C) 1991-2016 Altera Corporation. All rights reserved.
168.         // Your use of Altera Corporation's design tools, logic functions
169.         // and other software and tools, and its AMPP partner logic
170.         // functions, and any output files from any of the foregoing
171.         // (including device programming or simulation files), and any
172.         // associated documentation or information are expressly subject
173.         // to the terms and conditions of the Altera Program License
174.         // Subscription Agreement, the Altera Quartus Prime License Agreement,
175.         // the Altera MegaCore Function License Agreement, or other
176.         // applicable license agreement, including, without limitation,
177.         // that your use is for the sole purpose of programming logic
178.         // devices manufactured by Altera and sold by Altera or its
179.         // authorized distributors. Please refer to the applicable
180.         // agreement for further details.
181.
182.         // PROGRAM      "Quartus Prime"
183.         // VERSION      "Version 16.0.0 Build 211 04/27/2016 SJ Lite Edition"
184.         // CREATED      "Tue Mar 27 03:01:29 2018"
185.
186.         module lab1_registerfile
187.             #(parameter W = 8)
188.             (
189.                 we,
190.                 clk,
191.                 reset,
192.                 in,
193.                 sel1,
194.                 sel2,

```

```

195.         sel_dest,
196.         out1,
197.         out2
198.     );
199.
200.
201.     input wire  we;
202.     input wire  clk;
203.     input wire  reset;
204.     input wire [W-1:0] in;
205.     input wire [1:0] sel1;
206.     input wire [1:0] sel2;
207.     input wire [1:0] sel_dest;
208.     output wire [W-1:0] out1;
209.     output wire [W-1:0] out2;
210.
211.     wire    SYNTHESIZED_WIRE_0;
212.     wire    SYNTHESIZED_WIRE_1;
213.     wire    SYNTHESIZED_WIRE_2;
214.     wire    SYNTHESIZED_WIRE_3;
215.     wire    SYNTHESIZED_WIRE_4;
216.     wire    SYNTHESIZED_WIRE_5;
217.     wire    [W-1:0] SYNTHESIZED_WIRE_20;
218.     wire    [W-1:0] SYNTHESIZED_WIRE_21;
219.     wire    [W-1:0] SYNTHESIZED_WIRE_22;
220.     wire    [W-1:0] SYNTHESIZED_WIRE_23;
221.     wire    [W-1:0] SYNTHESIZED_WIRE_10;
222.     wire    [W-1:0] SYNTHESIZED_WIRE_11;
223.     wire    [W-1:0] SYNTHESIZED_WIRE_14;
224.     wire    [W-1:0] SYNTHESIZED_WIRE_15;
225.     wire    SYNTHESIZED_WIRE_18;
226.     wire    SYNTHESIZED_WIRE_19;
227.
228.
229.
230.
231.
232.     Decoder2to4 b2v_inst(
233.         .input0(sel_dest[0]),
234.         .input1(sel_dest[1]),
235.         .o0(SYNTHESIZED_WIRE_2),
236.         .o1(SYNTHESIZED_WIRE_3),
237.         .o2(SYNTHESIZED_WIRE_4),
238.         .o3(SYNTHESIZED_WIRE_5));
239.
240.
241.     Reg_WE b2v_inst10(
242.         .clk(clk),
243.         .reset(reset),
244.         .we(SYNTHESIZED_WIRE_0),
245.         .data(in),
246.         .out(SYNTHESIZED_WIRE_22));
247.     defparam b2v_inst10.W = W;
248.
249.
250.     Reg_WE b2v_inst11(
251.         .clk(clk),
252.         .reset(reset),
253.         .we(SYNTHESIZED_WIRE_1),
254.         .data(in),
255.         .out(SYNTHESIZED_WIRE_23));
256.     defparam b2v_inst11.W = W;
257.
258.     assign SYNTHESIZED_WIRE_18 = we & SYNTHESIZED_WIRE_2;
259.
260.     assign SYNTHESIZED_WIRE_19 = we & SYNTHESIZED_WIRE_3;

```

```

261.
262.     assign SYNTHESIZED_WIRE_0 = we & SYNTHESIZED_WIRE_4;
263.
264.     assign SYNTHESIZED_WIRE_1 = we & SYNTHESIZED_WIRE_5;
265.
266.
267.     Mux2to1 b2v_inst2(
268.         .select(sel1[0]),
269.         .i0(SYNTHESIZED_WIRE_20),
270.         .i1(SYNTHESIZED_WIRE_21),
271.         .out(SYNTHESIZED_WIRE_10));
272.     defparam b2v_inst2.W = W;
273.
274.
275.     Mux2to1 b2v_inst3(
276.         .select(sel1[0]),
277.         .i0(SYNTHESIZED_WIRE_22),
278.         .i1(SYNTHESIZED_WIRE_23),
279.         .out(SYNTHESIZED_WIRE_11));
280.     defparam b2v_inst3.W = W;
281.
282.
283.     Mux2to1 b2v_inst4(
284.         .select(sel1[1]),
285.         .i0(SYNTHESIZED_WIRE_10),
286.         .i1(SYNTHESIZED_WIRE_11),
287.         .out(out1));
288.     defparam b2v_inst4.W = W;
289.
290.
291.     Mux2to1 b2v_inst5(
292.         .select(sel2[0]),
293.         .i0(SYNTHESIZED_WIRE_20),
294.         .i1(SYNTHESIZED_WIRE_21),
295.         .out(SYNTHESIZED_WIRE_14));
296.     defparam b2v_inst5.W = W;
297.
298.
299.     Mux2to1 b2v_inst6(
300.         .select(sel2[1]),
301.         .i0(SYNTHESIZED_WIRE_14),
302.         .i1(SYNTHESIZED_WIRE_15),
303.         .out(out2));
304.     defparam b2v_inst6.W = W;
305.
306.
307.     Mux2to1 b2v_inst7(
308.         .select(sel2[0]),
309.         .i0(SYNTHESIZED_WIRE_22),
310.         .i1(SYNTHESIZED_WIRE_23),
311.         .out(SYNTHESIZED_WIRE_15));
312.     defparam b2v_inst7.W = W;
313.
314.
315.     Reg_WE b2v_inst8(
316.         .clk(clk),
317.         .reset(reset),
318.         .we(SYNTHESIZED_WIRE_18),
319.         .data(in),
320.         .out(SYNTHESIZED_WIRE_20));
321.     defparam b2v_inst8.W = W;
322.
323.
324.     Reg_WE b2v_inst9(
325.         .clk(clk),
326.         .reset(reset),

```



```

327.         .we(SYNTHESIZED_WIRE_19),
328.         .data(in),
329.         .out(SYNTHESIZED_WIRE_21));
330.         defparam      b2v_inst9.W = W;
331.
332.
333.     endmodule
endmodule

```

testbench:

```

1. module lab1_registerfile_tb
2.     #(parameter W = 3) ();
3.
4.     reg we,clk,reset;
5.     reg [1:0] sel1,sel2,sel_dest;
6.     reg [W-1:0] in;
7.     wire [W-1:0] out1,out2;
8.
9.     reg [16:0] mem [6:0];
10.
11.     lab1_registerfile DUT (we, clk, reset,in,sel1,sel2,sel_dest,out1,out2);
12.
13.     integer i,j;
14.
15.     initial begin
16.         clk=0;
17.         $readmemb("C:/Users/AhmetSalih/Desktop/EE446_Desktop/test_vectors/lab1_regis
terfile_tb_vector.txt" , mem);
18.         #1000;
19.     end
20.     always @* begin
21.         for(j=0;j<100;j=j+1) begin
22.             clk = clk ^ 1'b1;
23.             #5;
24.             //For now the frequency is too high but it's just for simulation
25.         end
26.     end
27.     always @*
28.     begin
29.         for(i=0;i<7;i=i+1) begin
30.             we = mem[i][16];
31.             reset = mem[i][15];
32.             in = mem[i][14:12];
33.             sel1 = mem[i][11:10];
34.             sel2 = mem[i][9:8];
35.             sel_dest = mem[i][7:6];
36.             #10;
37.             if({out1,out2} == mem[i][5:0])
38.                 $display ("No Error in %1d th row", i+1);
39.             else
40.                 $display ("Error in %1d th row", i+1);
41.         end
42.     end
43. endmodule

```

testvector:

```


1. //we_reset_in_sel1_sel2_sel_dest_out1_out2);
2. 1_1_101_10_11_10_000_000
3. 1_0_101_10_00_00_000_101

```

4. 1_0_111_11_01_01_000_111
5. 1_0_001_11_10_10_000_001
6. 1_0_011_11_11_11_011_011
7. 1_0_010_01_10_11_111_001
8. 1_1_001_10_11_01_000_000

1.4) Datapath

Schematics:

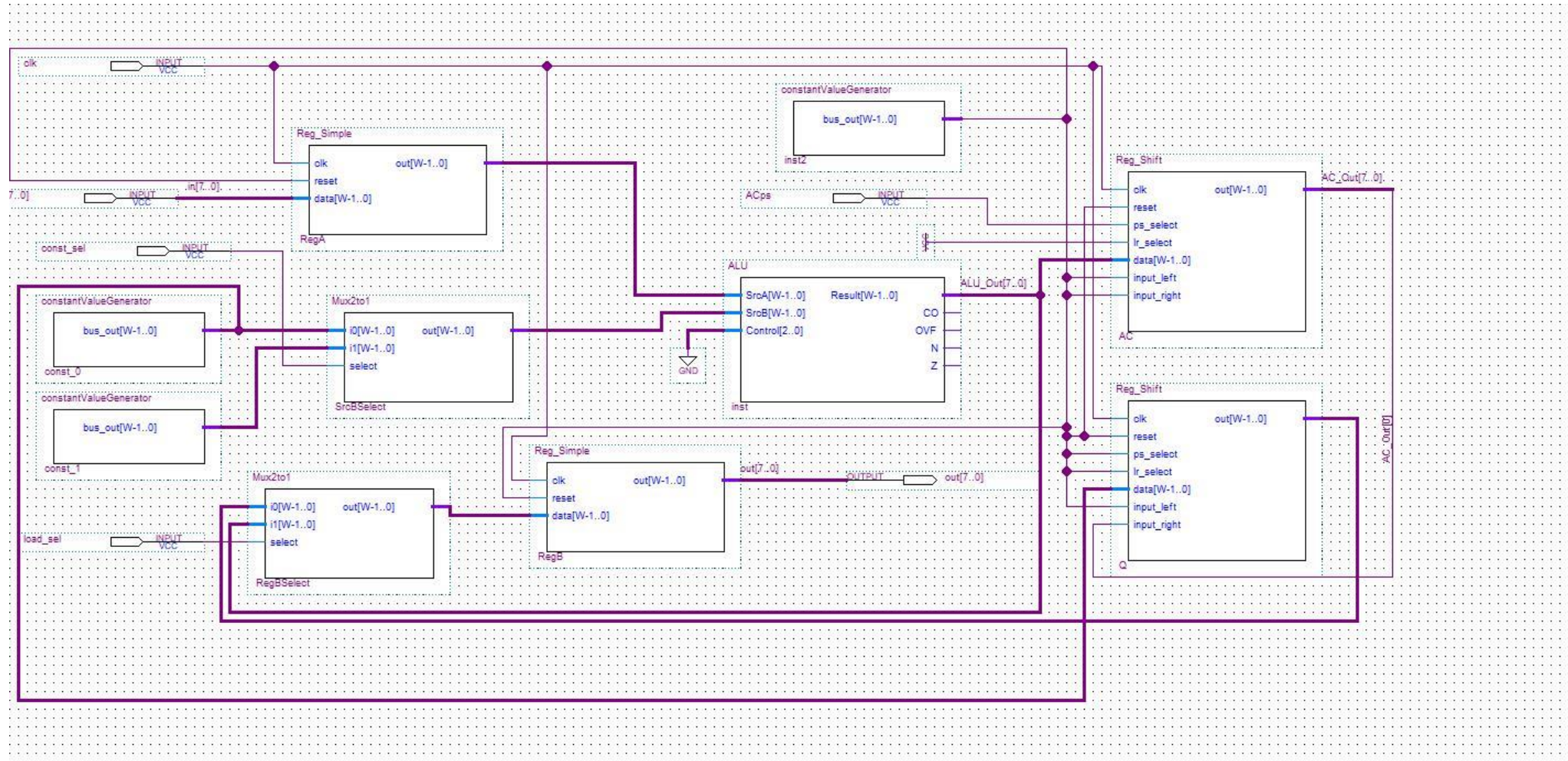

Q1) There are 3 control pins namely:

- const_sel (For the 2x1 MUX that selects the constant that goes to ALU)
- load_sel (For the 2x1 MUX that decides the input of RegB)
- ACps (AC register's parallel/serial select. First it has to load parallel then do serial computation)

Q2) There are 13 control signals in my architecture, including the reset signals. However 8 of those signals does not change over time. They also do not have to be changed for different instructions. For example ALU always does add operation so ALU's control signal is always 00, we also do not do any resetting so resets are always zero etc.

Q3) The 3 control pins is the minimum you can get. I have already reduced the number by inserting constant zeros and ones to unchanging pins. However,

- const_sel has to change for different instructions. LOAD and REVERSE LOAD requires 0 as constant, whereas INCREMENTED LOAD requires 1.
- load_sel has to change for different instructions. For LOAD and INCREMENTED LOAD operations it should select ALU's output as source. For REVERSE LOAD, it should select register Q's output as source.
- ACps has to change over time when the REVERSE LOAD instruction is executed. At first AC has to parallel load the data from ALU's output, but then it has to shift it one by one towards reg Q.

Q4) It takes 10 cycles:

Through all cycles const_sel=0 and load_sel=0(Q's output as source).

1st cycle: ACps=1 => AC Loads the data parallel

2-9 cycles: ACps=0 => AC shifts the data to right. Q shifts the to left. AC_Out[0] is connected as input_right to Q. This way the data is reversed in 8 cycles.

10th cycle ACps=X => RegB Loads the correct reversed data.